الدورة الشتوية لعام 2013

التخصص: إلكترونيات الطيران

يتكون هذا الاختبار من ( 100) سؤال موضوعي من نوع الاختيار من متعدد، الإجابة عنها إجبارية. ظلل بقلم الرصاص بشكل غامق الدائرة التي تشير إلى الإجابة الصحيحة في المكان المخصص لذلك في نموذج الإجابة المرفق.

### الاجهزة والدارات الالكترونية1

- 1. A silicon diode measures a high value of resistance with the meter leads in both positions. The trouble, if any, the diode is:
  - a- open

b- shorted to ground

c- internally shorted

d- ok

2. A reverse-biased diode has the\_\_\_\_\_ connected to the positive side of the source, and the \_\_\_\_\_ connected towards the negative side of the source.

a- cathode, anode

b- cathode, base

c- base, anode

d- anode, cathode

3. In an NPN transistor, the majority carriers in the base are:

a- free electrons

b- holes

c- neither

d- both

4. The ripple frequency of a bridge rectifier is:


a- the same as the input frequency

b- double the input frequency

c- four times the input frequency

d- cannot be determined

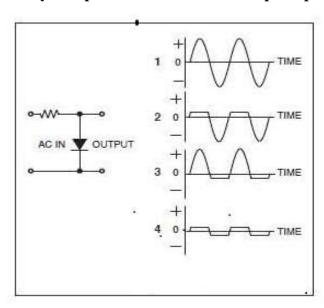5. With a pure AC signal input to the circuit shown in Figure below, what output wave form would you expect to see on an oscilloscope display?



a- 1

b- 2

c- 3

d- 4

6. The average value of the half-wave rectified output voltage is approximately \_\_\_\_ of Vp.

a- 31.8%

b- 63.6%

c- 70.7%

d- 100%

الدورة الشتوية لعام 2013

# 7. When the source voltage increases in a Zener regulator, which of these currents remains approximately constant?

a- Series current

b- Zener current

c- Load current

- d- Total current
- 8. Refer to Figure below. The symbol is for:




a- a triac

b- a UJT

c- a diac

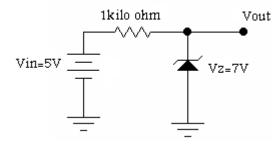- d- an SCR
- 9. The capacitance of a varactor diode:
  - a- remains constant as the bias voltage varies
  - b- decreases as the reverse bias voltage increases
  - c- increases as the reverse bias voltage increases
  - d- is usually 1000 μF or more
- 10. The output voltage for the circuit below is:



a- 5V

b- 2V


c- 7V

- d- Zero volts
- 11. In a transistor, the relation of the three transistor currents is:
  - a- Ic = IE + Pc

b- Ic = IB - 2IE

c-IE = Ic + IB

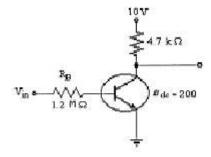- d-IC = IE + IB
- 12. Refer to the figure below. The value of Ic at cut off is:



a- 10.56 mA

b- 2.13 mA

c- 0.68 mA

d- equal zero

13. In a transistor, collector current is controlled by:

a- collector voltage

b- collector resistance

c- base current


d- all of the above

14. Saturation and cutoff are operating conditions that are very useful when operating the transistor:

a- as a linear amplifier

- b- as a switch
- c- as a current amplifier
- d- none of the above

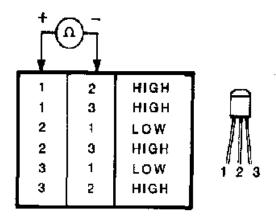15. The information in the chart below indicates that the transistor is a/an:



- a- NPN type and that lead 1 is the base lead.
- b- PNP type and lead 1 is the base lead.
- c- NPN type and lead 2 is the base lead.
- d- PNP type and lead 2 is the base lead.

16. A thyristor can be used as:


a- a resistor

b- an amplifier

c- a switch


d- a power source

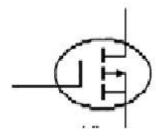17. Refer to Figure below. This symbol identifies:



- a- a P-channel E MOSFET
- b- an N-channel D MOSFET
- c- a P-channel D MOSFET
- d- an N-channel E MOSFET

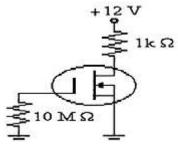
## 18. Refer to Figure below. If ID = 4 mA, the value of VDS IS:



- a- 12 V
  - 4 3 7
- c- 4 V

- b- 8 V
- d- 0 V
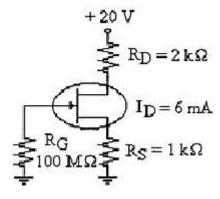
## 19. Refer to Figure below. The value of the voltage drop across RD is:



a- 20 V

b- 12 V

c- 6 V

d- 3 V

#### 20. The gate-source junction of a JFET is:

- a- normally not biased
- b- normally forward biased
- c- normally reverse biased
- d- a low resistance path for dc current when reverse biased

#### الهوائيات

## 21. The SWR on a transmission line is infinity, the line is terminated in:

- a- a complex impedance
- b- a short circuit

c- a pure reactance

d- a pure Resistance

#### 22. The velocity factor of a transmission line

- a- is higher for a solid dielectric than for air
- b- increases the velocity along the transmission line
- c- depends on the dielectric constant of the material used
- d- is zero if Zo=ZL

#### 23. High-frequency waves are:

- a- reflected by the D layer, night time
- b- absorbed by the f 2 layer
- c- non affected by the solar cycle
- d- reflected by the F layer, night time

#### 24. Diffraction of electromagnetic waves

- a- may occur around the edge of a sharp obstacle
- b- is caused by reflections from the ground
- c- arises only with spherical wave fronts
- d- is caused by refraction from the ionosphere

## 25. The antenna radiation of energy is more efficient when

- a- the time intervals between +Ve and Ve half cycles is short
- b- the time intervals between +Ve and Ve half cycles is long
- c- the mid- point impedance is more capacitive
- d- the mid- point impedance is more inductive

#### 26. The coaxial transmission lines are termed unbalanced since:

- a- they increase the power losses
- b- they match the load to the source
- c- they have one grounded conductor
- d- they have two grounded conductors

## 27. When the two components of electric field are equal in magnitude, the electromagnetic wave polarization is

- a- elliptical
- b- spherical

c- circular

d- horizontal

#### 28. The skip distance is:

- a- the distance within which the wave can be received
- b- the minimum available distance required to make communication
- c- the maximum required distance to make communication
- d- the distance between the transmitter and the receiver

#### 29. Which of the following terms does not apply to the Yagi-array:

a- parabolic antenna

- b- folded dipole
- c- Bi- directional radiation
- d- balance load

#### 30. Horn feed is used with a parabolic reflector to

- a- increase the gain of the system
- b- increase the beam width of the system
- c- reduce the size of the reflector
- d- reduce the size of the director

## 31. To build $\lambda/2$ dipole to receive a 100MHz broadcast, the actual optimum physical length of the antenna must be:

a- 1.43 meter

b- 2.57 meter

c- 5 meter

d- 5.7 meter

## 32. If a frequency of a signal is $3\times10^{14}$ Hz, then its wave length is:

a- 1 micro-meter

b- 1 meter/second

c- 1 milli-meter

d- 1 meter

الدورة الشتوية لعام 2013

## 33. Characteristic impedance $Z_0$ for a transmission line is given by:

a- 
$$Z_0 = \sqrt{\frac{L}{C}}$$
 ohms

b- 
$$Z_o = \sqrt{\frac{1}{LC}}$$
 ohms

c- 
$$Z_0 = \sqrt{\frac{C}{L}}$$
 ohms

d- 
$$Z_o = \frac{1}{2\pi LC}$$
 ohms

## 34. The quarter-wave antenna generally:

- has one  $\frac{\lambda}{4}$  pole with earth ground instead of the missing quarter wave
- b- has one  $\frac{\lambda}{2}$  pole with earth ground instead of the missing quarter wave
- c- has one  $\lambda$  pole with earth ground instead of the missing quarter wave
- d- has  $2\lambda$  pole with earth ground instead of the missing quarter wave

## 35. Higher frequency waves have:

a- shorter wave length

- b- longer wave length
- c- medium wave length
- d- variable wave length

## 36. Radio waves is propagated by sky wave:

- a- from the ionosphere
- b- from the troposphere
- c- in or close to earth
- d- in far to earth

## 37. The troposphere thick is about:

a- 10 miles

b- 20 miles

c- 30 miles

d- 40 miles

## 38. The angle between electric and magnetic fields in a wave guide is:

a- 90°

b- 0°

c- 180°

d- 360°

## 39. Impedance inversion may be obtained with:

a- a half wave line

b- a quarter- wave line

c- short-circuited stub

d- an open-circuited stub

## 40. Frequencies in the UHF range propagate by means of:

a- space waves (LOS)

- b- sky waves
- c- surface waves (HOS)
- d- ground waves

## الدارات النبضية

#### 41. The square wave consist of:

a- Odd harmonics

- b- Even harmonics
- c- Fundamental frequency
- d- Odd harmonics +even harmonics

### 42. In the integrated LR circuit the output will be taken across the:

a- Capacitor

b- Resistor

c- Diode

d- Inductor

الدورة الشتوية لعام 2013

التخصص: إلكترونيات الطيران

## 54. The output frequency of a Bistable multivibrator is:

a- Double the input frequency

b- One half of the input frequency

c- Equals the input frequency

d- None of the above

### 55. Which of the following pulses is used to change states in a flip flop?

a- A trigger pulse


b- A clipping pulse

c- A modulating pulse

d- An interference pulse
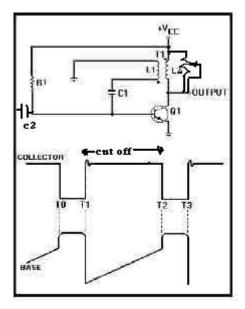
## **Blocking oscillator**

\*\*\*\* In answering questions 56 through 60, refer to figure 1



56. The blocking oscillator is a special type of wave generator used to produce:

a- square wave

b- Sawtooth wave

c- Narrow pulse

d- Non of the above

57. If the frequency of the external trigger is 4kHz, & the free running frequency is 3kHz, then the out put frequency will be:

a- 12kHz

b- 4kHz

c- 3kHz

d- 7kHz

58. The parameters that determine the long of cut off region are:

a- L1,Rc

b- L1,C1.

c- C1,R1.

d- L1,R1.

59. The component that used to over come the over shoot is:

a- L2

b- Opposite polarity of L1 & L2

c- Variable R2

d- R1

60. The parameters that determine the pulse width are:

a- L2,R2

b- L2,L1

c- L1,R1

d- L1,Rc

## المعالجات الدقيقة

61.	The instruction STA 5060h requires:						
	a-	1 byte	b-	2 bytes			
	c-	3 Bytes	d-	4 bytes			
<b>62.</b>	The	The flag register in 8085 microprocessor has:					
	a-	4 flags	b-	5 flags			
	c-	6 flags	d-	8 flags			
63.	Acc	cumulator is a part of:					
	a-	CU	b-	ALU			
	c-	Memory	d-	Timing unit			
64.	A register in the microprocessor that keeps track of the answer or results of arithmetic or logic operation is the:						
	a-	stack pointer	b-	program counter			
	c-	instruction pointer	d-	accumulator			
<b>65.</b>	A r	A register in the microprocessor which is involved with pop and push operations is:					
	a-	SP	b-	IP			
	c-	AC	d-	PC			
66.	The register which keeps the address of next instruction to be executed is:						
	a-	PC	b-	SP			
	c-	BP	d-	A			
<b>67.</b>	Clock is measured in:						
	a-	Bits per second	b-	baud			
	c-	Bytes	d-	Hertz			
68.	A n	A machine cycle refers to:					
	a-	fetching an instruction					
	b-	clock speed					
	c- fetching, decoding and executing an instruction						
	d-	executing an instruction					
69.	One of the addressing modes not used in M6800 microprocessor is:						
	a-	Direct	b-	Immediate			
	c-	Register Direct	d-	Register In-Direct			
70.	The address length in 8080 microprocessor is:						
	a-	2	b-	4			
	c-	8	d-	16			
71.	The number of data lines in 8080 microprocessor is:						
	a-	32	b-	20			
	c-	16	d-	8			

72. The circuits in the 8085A that provide the arithmetic and logic functions are called the:

a- CPU

b- ALU

c- ELU

d- CU

73. How many buses are connected as part of the 8080 microprocessor?

a- 8

b- 5

c- 3

d- 2

X Suppose we have the following memory:

1	LOAD	200
2	ADD	100

me	memory		
address	contents		
100	05		
101	201		
102	01		
200	100		
201	101		
202	102		

74. What will be in the accumulator after executing instruction 1 and 2:

a- 300

b- 501

c- 105

d- 101

75. Using question X what will be in the accumulator after executing instruction 1 and 2:

- 1 LOAD @200
- 2 ADD @101
- a- 201

b- 101

c- 05

d- 106

76. Using question X what will be in the accumulator after executing instruction 1, 2 and 3:

- 1 LOAD #100
- 2 ADD #200
- 3 STORE 100
- a- 10

b- 105

c- 200

d- 300

77. The 8080 is:

a- 16-bit parallel CPU

b- 8-bit serial CPU

c- 8-bit parallel CPU

d- 16-bit serial CPU

## 88. What are the principal frequencies that appear at the output of a mixer circuit?

- a- Two and four times the original frequency
- b- The sum, difference and square root of the input frequencies
- c- The original frequencies and the sum and difference frequencies
- d- 1.414 and 0.707 times the input frequency

# 89. A circuit that converts frequency or phase change into a DC voltage is called a/an:


a- AM converter

b- DC phasor

c- Phase detector

d- PLL

## 90. Calculate the modulation depth:

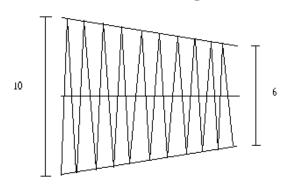

a- 0.6

b- 0.25

c- 1.67

- d- 125
- 91. The power dissipated by an amplitude modulated wave is 100 W when the depth of modulation is 40%.the modulation depth needed to increase the power to 120W is:
  - a- 64%

b- 77%

c- 60%

- d- 67%
- 92. The bandwidth of an FM system , when mf = 5 and  $\Delta f$  = 75 khz is equal to:
  - a- 140 kHz

b- 120 kHz

c- 180 kHz

- d- 90 kHz
- 93. The telephone signal has a frequency between 300 3400 Hz. The sampling frequency that represents this signal is:
  - a- 600 Hz

b- 3100 Hz

c- 6800 Hz

- d- 6200 Hz
- 94. One of the advantages of ASK over FSK is:
  - a- it needs less bandwidth
- b- it needs twice bandwidth
- c- it has two carrier signals
- d- it hasn't a carrier
- 95. In comparison between 2PSK and 4PSK with respect to the bandwidth needed:
  - a- 2PSK needs less bandwidth
  - b- 4PSK needs half the bandwidth
  - 4PSK needs double bandwidth
  - d- both need same bandwidth

96. The type of AM used for sound broadcasting is:


a- DSB-SC

b- JJB

c- DSB

d- VSB

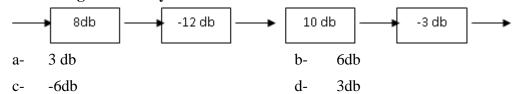97. The over gain of the system shown below is:



98. Am circuit used signal generator for?

- a- Broadcast transmitter
- b- Testing and alignment
- c- Generate square pulse
- d- None of the above

99. The length of the dipole in bi-directional antenna is:

a- 0.25λ

b- 0.5λ

c- λ

d- 1.5λ

100. The band frequency used in sky wave:

a- LF

b- VLF

c- HF

d- MF

انتهت الأسئلة